



Lab Report - 01

Course No: 206

Course Title: Digital Logic Design

Submitted To:

Iffat Tamanna

Dept: CSE

Submitted By:

Md: Zobayer Hasan Nayem

Id: 19202103274

Section: 07

Dept: CSE

Name of Experiment:

Verify the Behavior of Logic Gates using Truth Tables and Familiarization with Digital Logic Gate. on proteus

Logic Gates below:

Experiment Equipment

① OR Gate

Logic Gates

② AND Gate

Logic probe

③ NOT Gate

Logic state.

④ NOR Gate

⑤ NAND Gate

⑥ X-OR Gate

⑦ X-NOR Gate. Table for Truth & OR Gates

A	A
1	0
0	1

$X = A + B$

input		output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1




Q2

Truth table for AND Gates

$$X = A \cdot B$$

Input		
A	B	$X = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1
		output

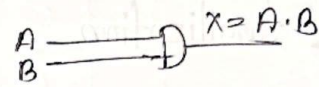

Truth table of NOT Gate

$$X = \overline{A}$$

A	$X = \overline{A}$
0	1
1	0





X	A	B
0	0	0
1	1	0
1	0	1
1	1	1

Truth Table for NOR Gate

③

$$X = \overline{A+B}$$



A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

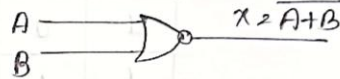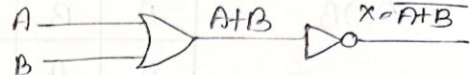

Truth table for NAND GATE

$$X = \overline{A \cdot B}$$

A	B	A · B	$\overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

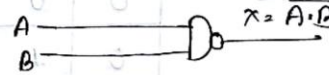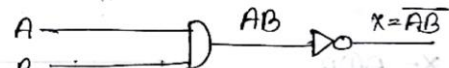

(4)

Truth Table for x-OR Gate

$$X = A \oplus B$$

$$= \bar{A}B + A\bar{B}$$


A	B	\bar{A}	\bar{B}	$\bar{A}B$	$A\bar{B}$	$\bar{A}B + A\bar{B}$
0	0	1	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0

Truth Table for x-NOR Gate




$$X = A \oplus B$$




$$= AB + \bar{A}\bar{B}$$


A	B	\bar{A}	\bar{B}	AB	$\bar{A}\bar{B}$	$AB + \bar{A}\bar{B}$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

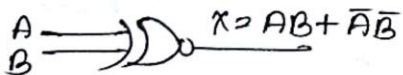

All Logic Gates

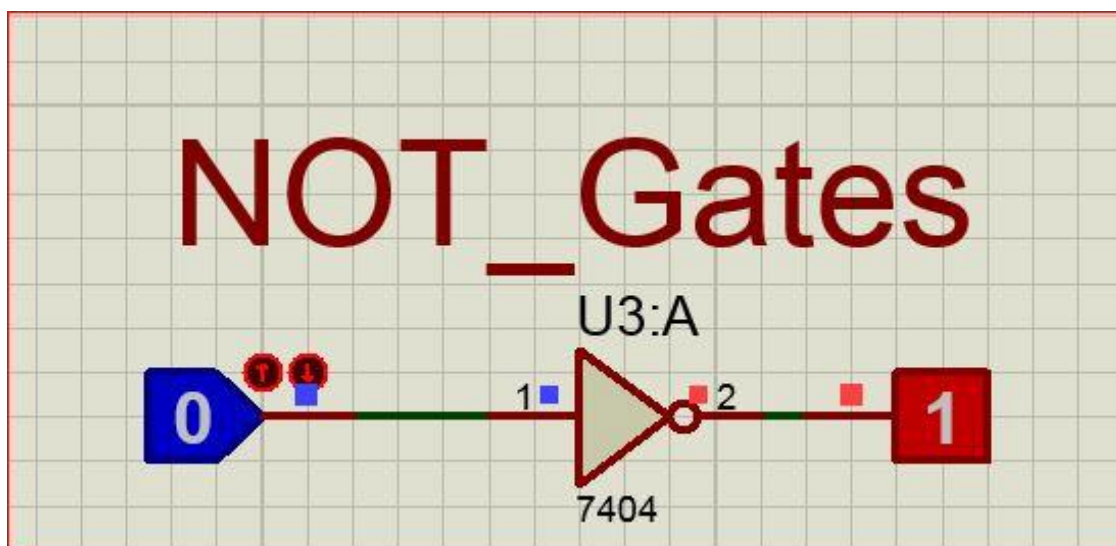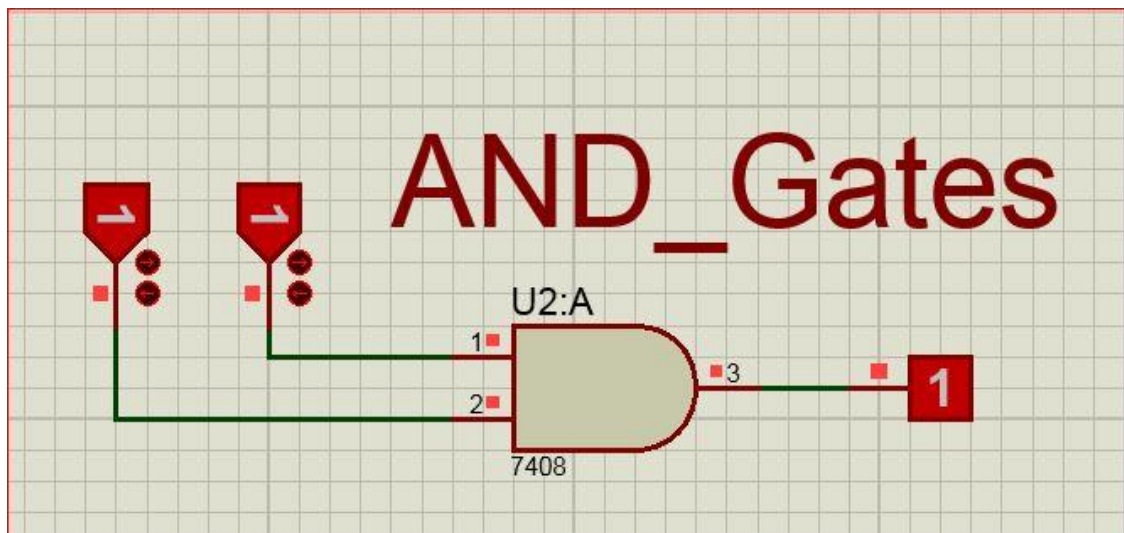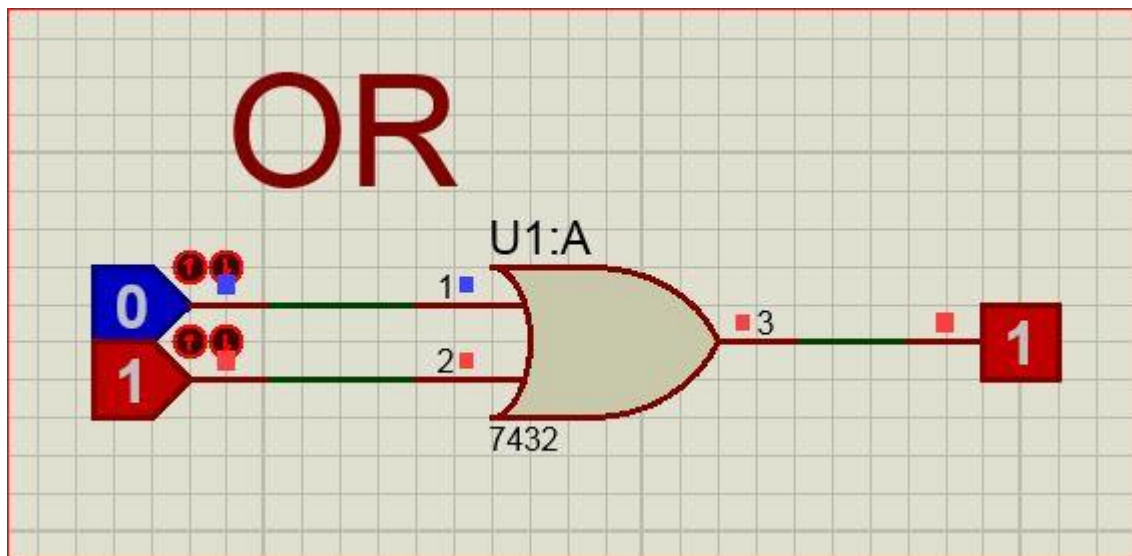

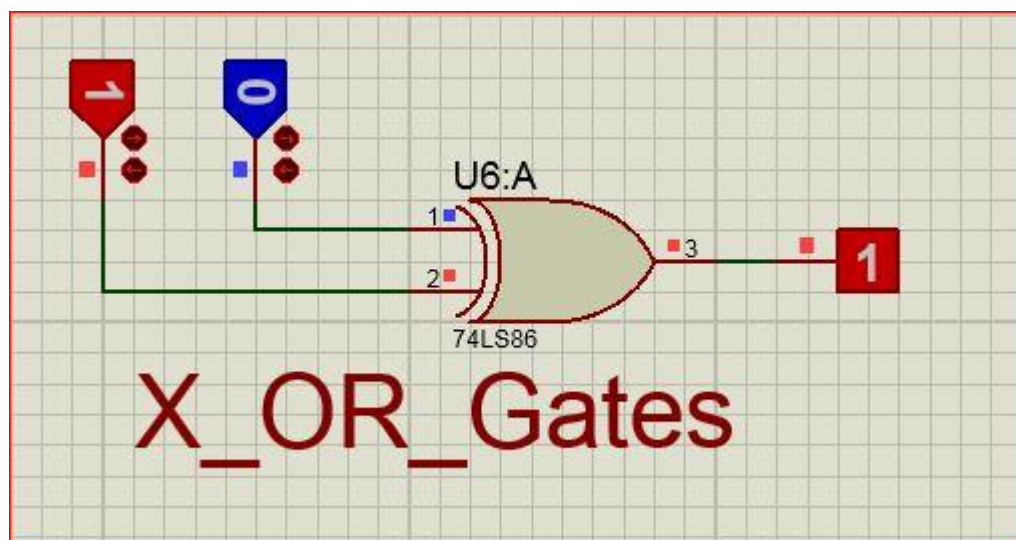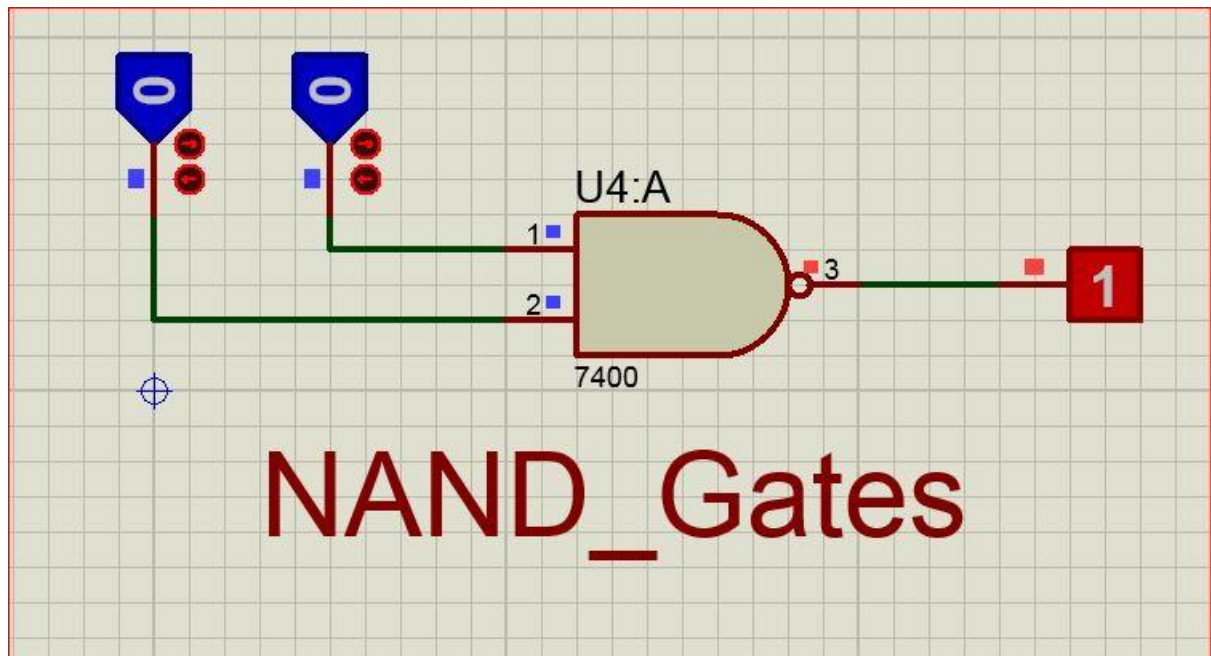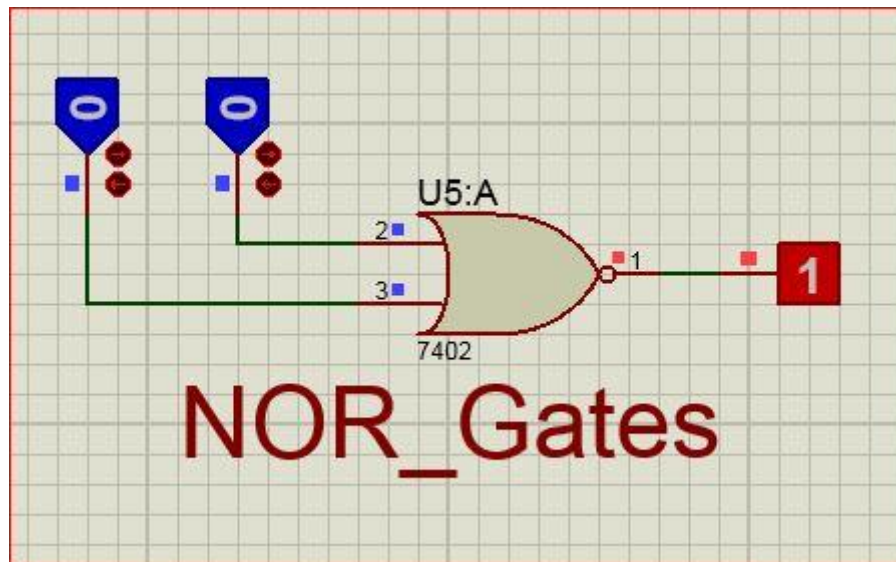

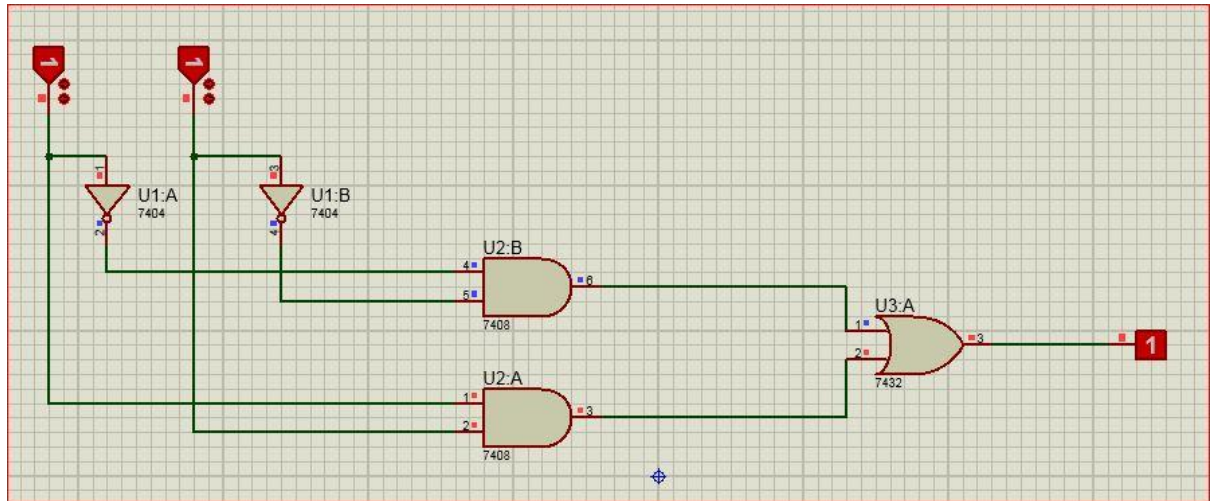

Picture of X_NOR Gates

Conclusion :

1. we have learnt how to implement circuits in proteus software.
2. we have understood the digit simulation of any circuit in the software.
3. we have verified the truth table for each input/output combination.
4. we repeated the process for all others logic gates.