



Lab Report - 05

Course No: 206

Course Title: Digital Logic Design

Submitted To:

Iffat Tamanna

Dept: CSE

Submitted By:

Md: Zobayer Hasan Nayem

Id: 19202103274

Section: 07

Dept: CSE

Lab Report → 05

ID: 19202103274

Name of Experiment: Contrast and test combination

Logic circuit parity generator.

Equipment:

1. 8 input OR gate
2. 4 input AND gate
3. Not gate
4. Logic probe
5. Logic state

Description: A parity Bit is a Bit added to a string of Binary code. parity bit are a simple form of error detecting code. parity Bit are generally applied to the smallest units of a communication protocol, typically 8-bit octets (bytes). although they can also be applied separately to an entire message string of bits. The parity bit ensure that

the total numbers of 1-bits in the string is even or odd. There are two variants of parity bit: even parity bit and odd parity bit.

Even parity: parity bit are added to transmitted message to ensure that the numbers of bit with a value of one in a set of bits add up to even or odd numbers. Even and odd parities are the two variants of parity checking modes. even parity can be more clearly explained by means of an example. Consider the transmitted message 1010001, which has three ones in it. This turned into even parity by adding a one, making the sequence 1 1010001, so that there are four ones (an even number). If the transmitted message has the form 1101001, which is already an even number, a zero is added to sustain the even parity.

Even parity

This is the truth table of Even parity.


w	x	y	z	Even parity
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Re-map

$wx \backslash yp$	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0

$$F = w'x'y'p + w'x'yp' + w'xy'p' + w'xyp + wxy'p + wx'y'p' + wxy'p' + wx'yp$$

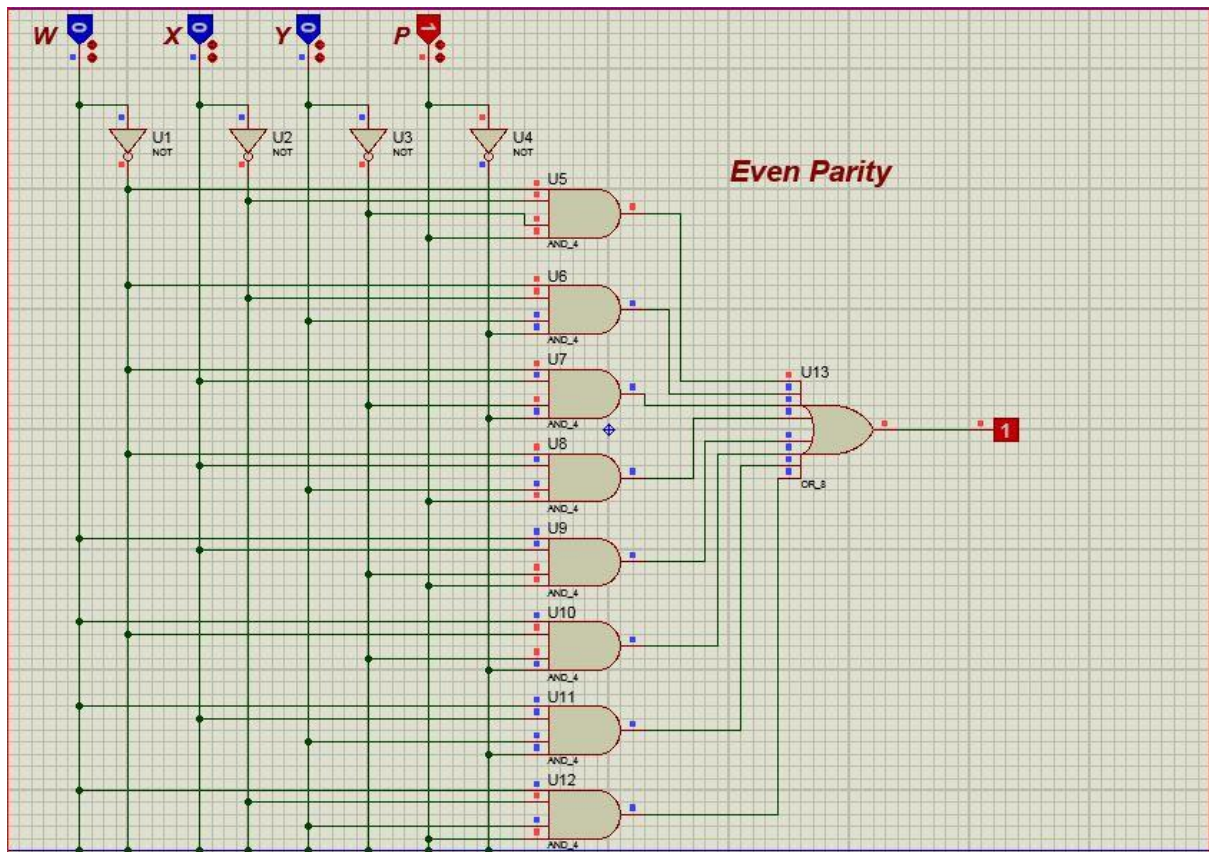I will design the circuit in proteus software.



odd parity: odd parity can be more clearly explained

through an example. Consider the transmitted message

1010001, which has three ones in it. This is

turned into odd parity by adding a zero, making

the sequence 01010001. Thus, the total number

of ones remain at three, an odd number.

if the transmitted message has the form 1101001,

which has four ones in it, this can be turned

into odd parity by adding a one, making

the sequence 11101001.


0	1	0	1	1
0	1	0	1	1
0	0	1	1	1
1	1	1	1	1

K-map for odd parity

xy \ p	00	01	11	10
00	1	0	1	0
01	0	1	0	1
11	1	0	1	0
10	0	1	0	1

$$F = \bar{w}\bar{x}'y'p' + \bar{w}\bar{x}'yp + \bar{w}xy'p' + \bar{w}xyp' + \bar{w}xy'p + \bar{w}xyp + w\bar{x}'y'p' + w\bar{x}'yp + wxy'p' + wxyp' + wxy'p + wxyp$$
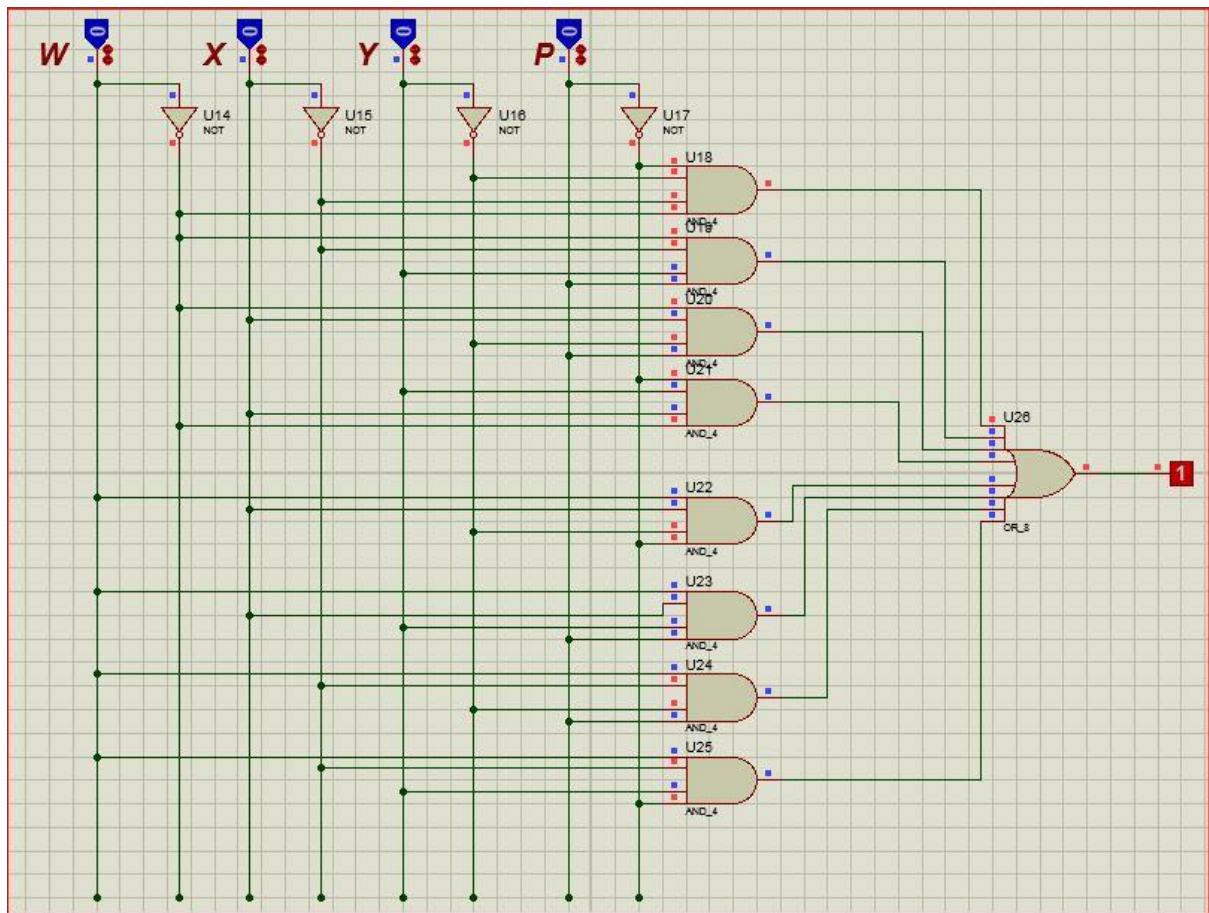
$$+ w\bar{x}'y'p' + w\bar{x}'yp + wxy'p' + wxyp'$$



Conclusion:

- ① we have learnt how to implement ~~odd~~ Even parity & odd parity.
- ② we also know how to work even & odd parity.
- ③ we also know odd parity wants to transmit 1001 and odd parity bit and sends 10011.
- ④ we also know even parity wants to transmit 1001 and odd parity bit and sends 10010.
- ⑤ we also know how to create function of parity Bit.

Name of Experiment: Design of code converters like BCD to Excess-3.

Describe: To understand the process of converting BCD to excess-3, it is required to have knowledge of numbers system and numbers base conversion. The excess-3 binary code is an example of a self-complementary BCD code. A self-complementary binary code is a code which is always complemented in itself. By replacing the bit 1 to 0 and 0 to 1 of a number. The sum of all the 1's complement and the binary numbers of a decimal is equal to the binary numbers of decimal 9.

The process of BCD to excess-3. The excess-3 code can be calculating added 3 (0011) to each BCD code.

Truth table

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

we will use the K-map method to design
and make function for the conversion of
BCD to Excess-3.

AB \ CP	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	x	x	x	x
10	1	1	x	x

$$w = A + BP + BC$$

AB \ CP	00	01	11	10
00		1	1	1
01	1	0	0	0
11	x	x	x	x
10	0	1	x	x

$$x = B'P + B'C + BC'P'$$

AB \ CP	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	x	x	x	x
10	1	0	x	x


$$y = C'P' + CP$$

AB \ CP	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	x	x	x	x
10	1	0	x	x

$$Z = p'$$

AB \ CP	00	01	11	10
00	1	1	1	1
01	0	0	0	1
11	x	x	x	x
10	0	1	x	x

AB \ CP	00	01	11	10
00	1	1	1	1
01	0	0	0	1
11	x	x	x	x
10	0	1	x	x

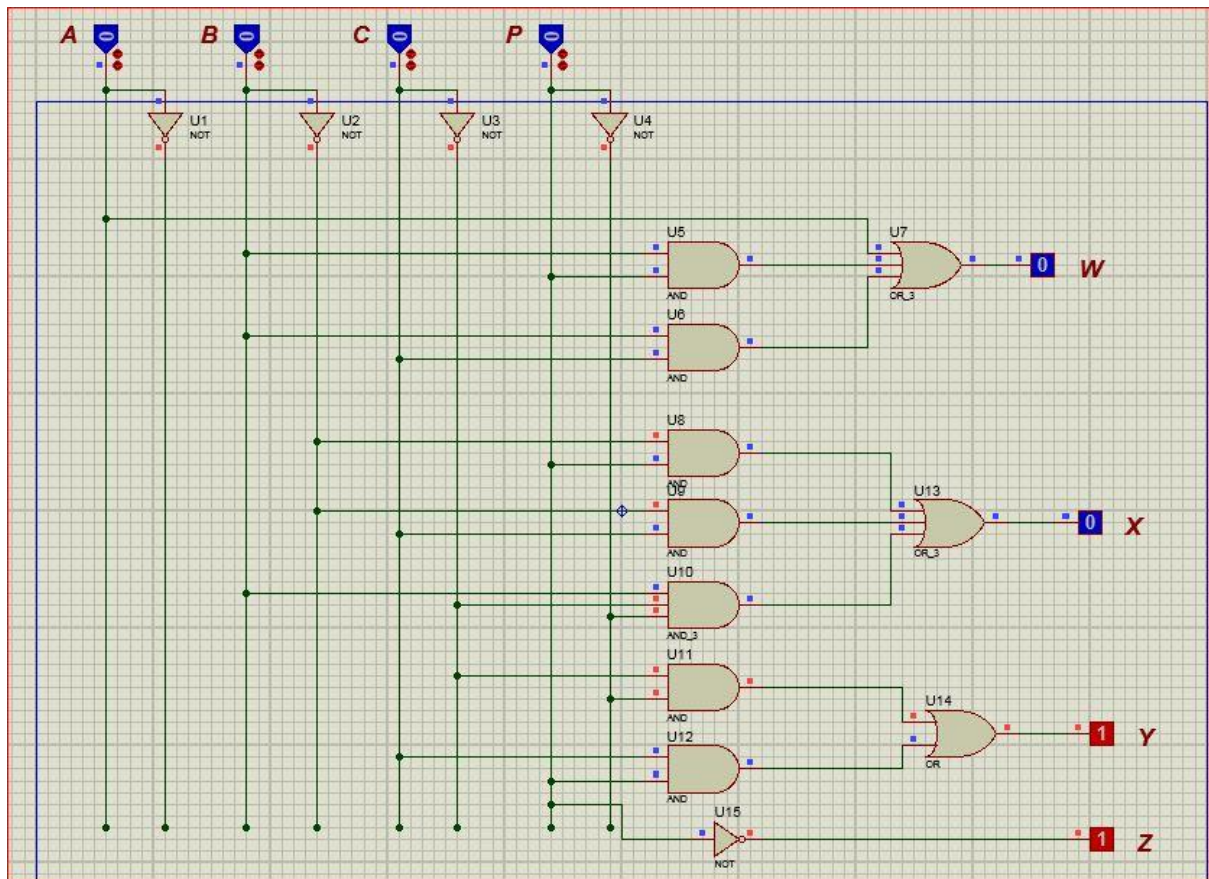

Conclusion:

- ① we have learnt how to convert BCD to Excess-3 code.
- ② we have learnt that how to implement Code.
- ③ we also learnt that how to use k-map using to the BCD to Excess-3 Code.

0	1	0	1	0
0	1	0	1	0
x	x	x	x	11
x	x	0	1	01