



# Lab Report - 06

Course No: 206

Course Title: Digital Logic Design

**Submitted To:**

Iffat Tamanna

Dept: CSE

**Submitted By:**

Md: Zobayer Hasan Nayem

Id: 19202103274

Section: 07

Dept: CSE

## Lab-06

Name of Experiment: To check the operation of 2 to 4 line Decoder / 3 to 8 line Decoder and design circuit.

Equipment:

1. 3 input AND Gate
2. Not Gate
3. Logic probe
4. Logic state

Description: A decoder is a circuit that changes a code into a set of signals. It is called a decoder because it does the reverse of encoding, but we will begin our study of ~~encoder~~ decoders.

A common type of decoder is the line decoder which takes an  $n$ -digit binary number and decodes into  $2^n$  data lines. The simplest is the 2 to 4 line decoder.

The truth table of 2 to 4 line decoder:

A	B	$D_0$	$D_1$	$D_2$	$D_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$D_0 = \overline{A} \overline{B}$$

$$D_1 = \overline{A} B$$

$$D_2 = A \overline{B}$$

$$D_3 = AB$$

### 3 to 8 line Decoder

In 3 to 8 line decoder, it includes three inputs and eight outputs. Here the inputs are represented through ~~three~~ A, B, C. whereas the output

are represented through  $D_0, D_1, D_2, \dots, D_7$

The selection of 8 output can be done based on three inputs.

Truth table of 3 to 8 line decoder

A	B	C	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$D_0 = \bar{A}\bar{B}\bar{C}$$

$$D_1 = \bar{A}\bar{B}C$$

$$D_2 = \bar{A}B\bar{C}$$

$$D_3 = \bar{A}BC$$


$$D_4 = A\bar{B}\bar{C}$$

$$D_5 = A\bar{B}C$$


$$D_6 = AB\bar{C}$$

$$D_7 = ABC$$

## 2 to 4 Deecoder

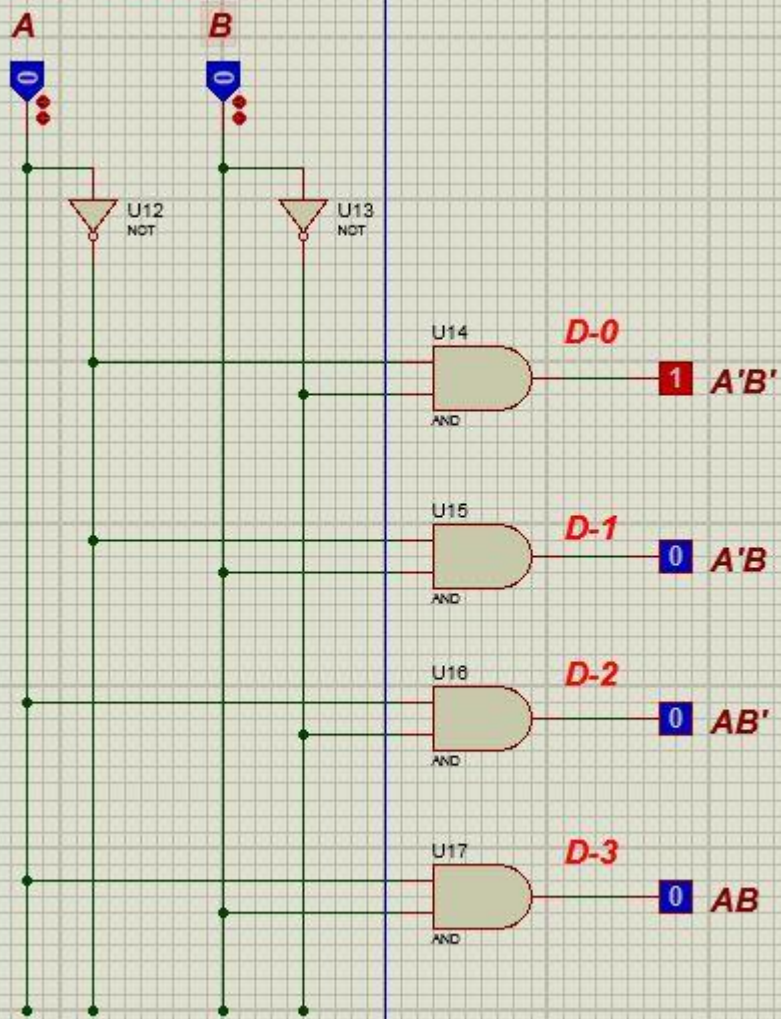



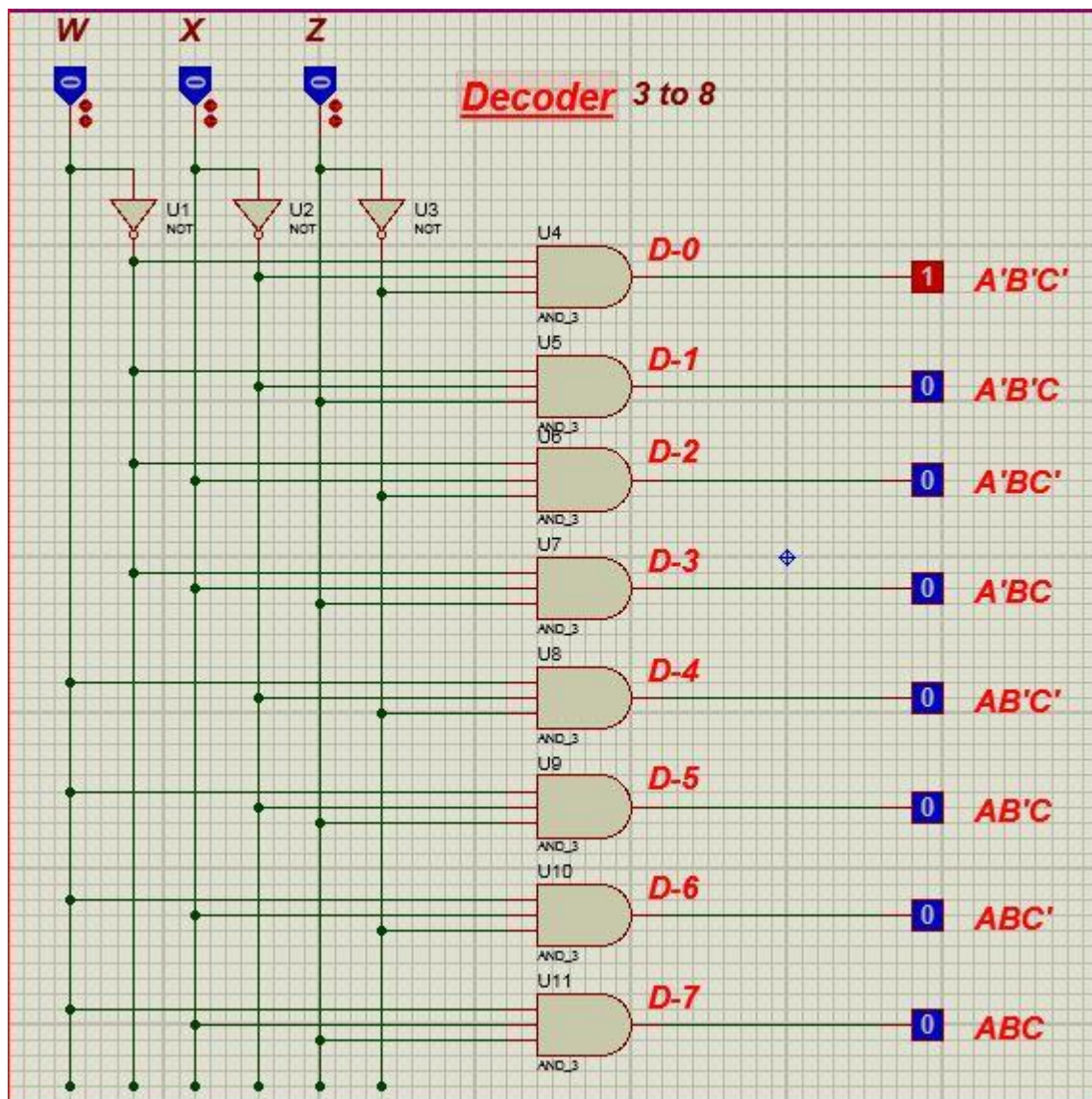

## Conclusion

- ① we have learnt that how to operate 2 to 4 line decoder.
- ② we have also learnt how to operate 3 to 8 line decoder.
- ③ we have learnt how to find out the relation between input and output of a decoder.
- ④ we have also learnt how to implement a circuit of decoder using Basic gates.

